


Ripple factor of Rectifiers

Ripple factor

The output of rectifier has dc component and ac component (referred as ripple)
we can define ripple factor as:

$$\begin{aligned}\text{Ripple factor} &= \frac{\text{rms value of ac component}}{\text{value of dc component}} \\ &= \frac{I_{ac}(\text{rms})}{I_{dc}} \quad \text{or} \quad \frac{V_{ac}(\text{rms})}{V_{dc}}\end{aligned}$$

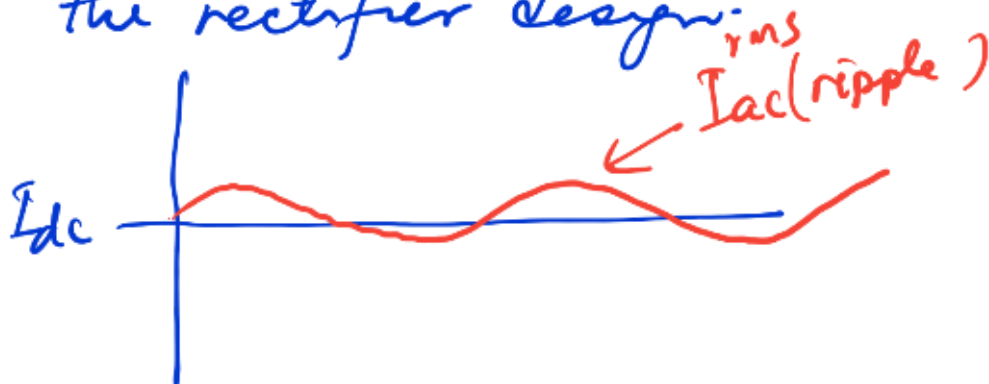Lower be the ripple factor, better will be the rectifier design.



effective rms value of total load current

$$I_{rms} = \sqrt{I_{dc}^2 + I_{ac}^2}$$

$$\begin{aligned}\text{ripple factor} &= \frac{I_{ac}}{I_{dc}} = \frac{1}{I_{dc}} \sqrt{I_{rms}^2 - I_{dc}^2} = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}\end{aligned}$$

For HW

$$I_{rms} = \frac{I_m}{2}, \quad I_{dc} = \frac{I_m}{\pi}$$

$$\text{ripple factor (HW)} = 1.21$$

For Full wave

$$I_{rms} = \frac{I_m}{\sqrt{2}}; \quad I_{dc} = \frac{2I_m}{\pi}$$

$$\begin{aligned} \text{ripple factor} &= \sqrt{\frac{(I_m/\sqrt{2})^2}{(2I_m/\pi)^2} - 1} \\ &= 0.48 \end{aligned}$$