

Name:	Kalahastri Likhith Sai Ganesh
Roll Number:	20IM10017


1. **Aim of the experiment:** Studies on small-signal CE amplifier

2. **Tools used:** Resistors, Capacitors, NPN Transistor, Voltage Source.

3. **Background knowledge (brief):**


A transistor is a type of **semiconductor** device that can be used to both conduct and insulate electric current or voltage. A transistor acts as a switch and an amplifier. There are three terminals for a transistor. They are:

- Base
- Collector
- Emitter

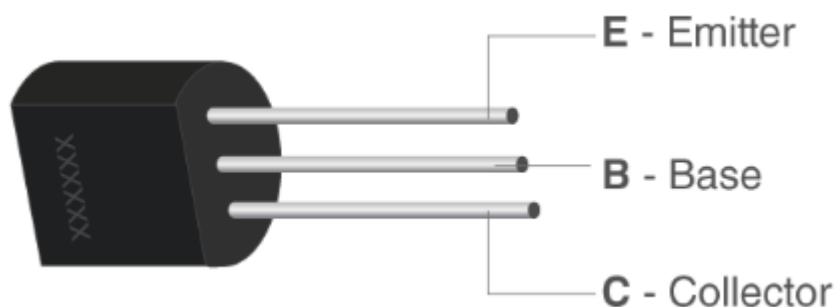


P-N-P Transistor: It is a type of BJT where one n-type material is introduced or placed between two p-type materials

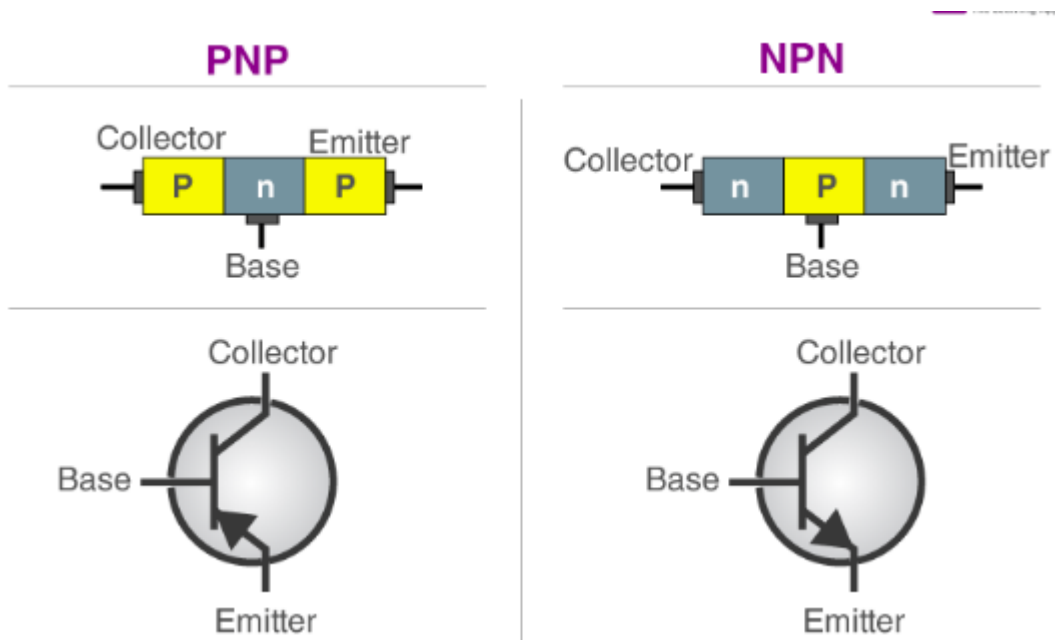
N-P-N Transistor: In this transistor, we will find one p-type material between two n-type materials.



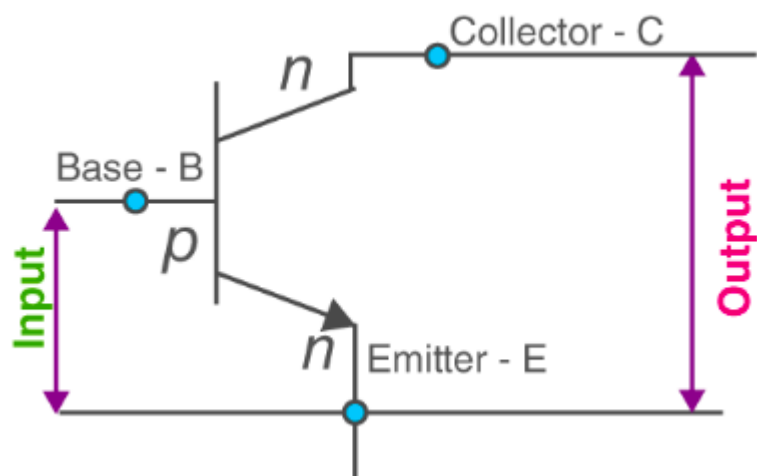In Common Emitter (CE) configuration, the emitter terminal is shared between the input and the output terminals.




Output Characteristics of a CE Amplifier

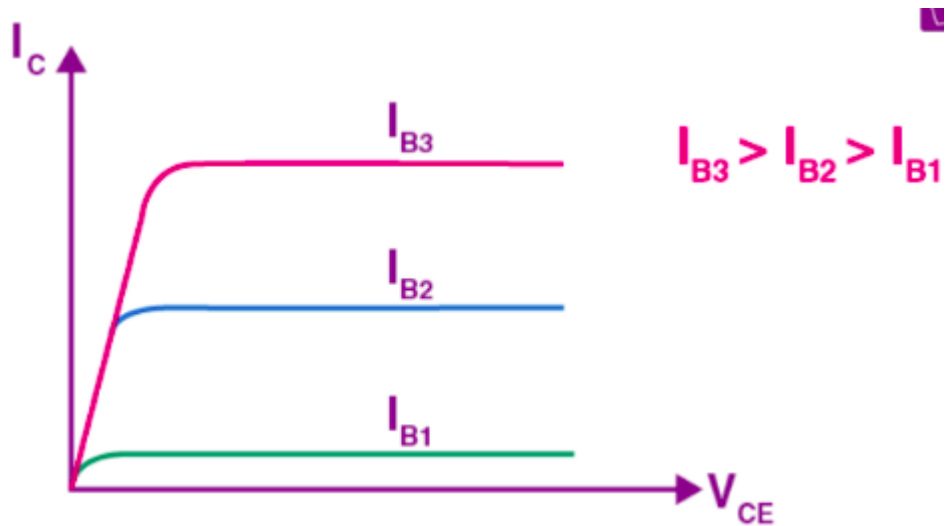


4. Circuit (hand drawn/image):

Measurement of DC conditions

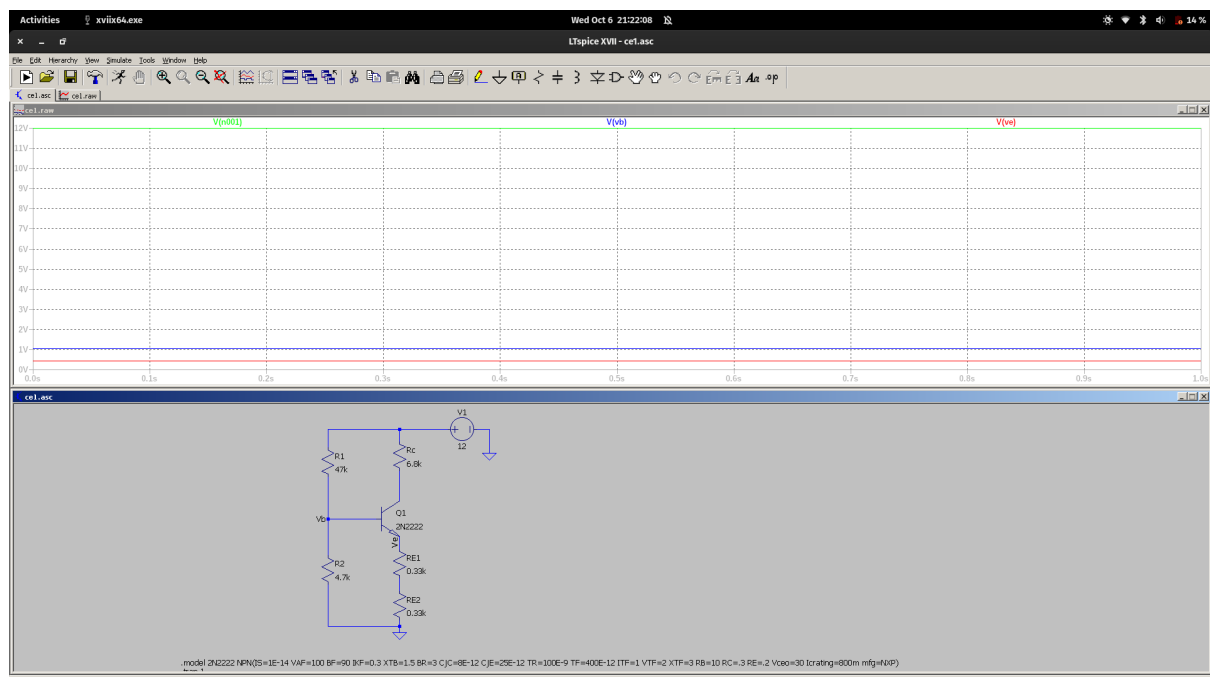

$$V_b = 1.0627V, V_c = 12V, V_e = 420.955mV$$

Measurement of DC conditions:-

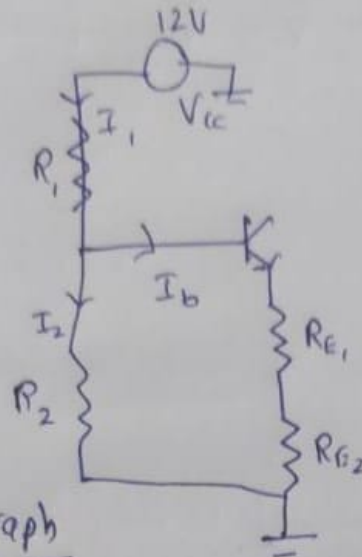

from graph

$$V_b = 1.0627 \text{ V}$$

$$I_1 = I_2 + I_b$$

$$V_e = 420.95 \text{ mV}$$

$$V_B = I_2 R_2$$

$$V_{be} = V_b - V_e = 0.641 \text{ V}$$

$$V_{ce} = V_c - V_e = 11.579 \text{ V}$$

$$I_2 = \frac{1.0627}{4700} = 0.2261 \text{ mA}$$

$$12 - I_1 R_1 = V_B$$

$$V_E - I_E (R_{E1} + R_{E2}) = 0$$

$$I_1 = \frac{12 - 1.0627}{47000}$$

$$I_E = \frac{420.95 \times 10^{-3}}{0.66 \times 1000}$$

$$\boxed{I_1 = 0.2327 \text{ mA}}$$

$$= 0.6378 \text{ mA}$$

$$I_b = I_1 - I_2 = -0.0066 \text{ mA}$$

$$I_e = I_c + I_b$$

$$I_c = I_e - I_b = 0.6378 + 0.0066 = 0.6444 \text{ mA}$$

From Calculations,


$V_{be} = 0.641745V$, $V_{ce} = 11.579V$, $I_c = 0.6444mA$, $I_e = 0.6378mA$

Signal Handling Capacity

$F = 4KHz$

1)Without Load Resistance -

a) $V_{in} = 0.1V$

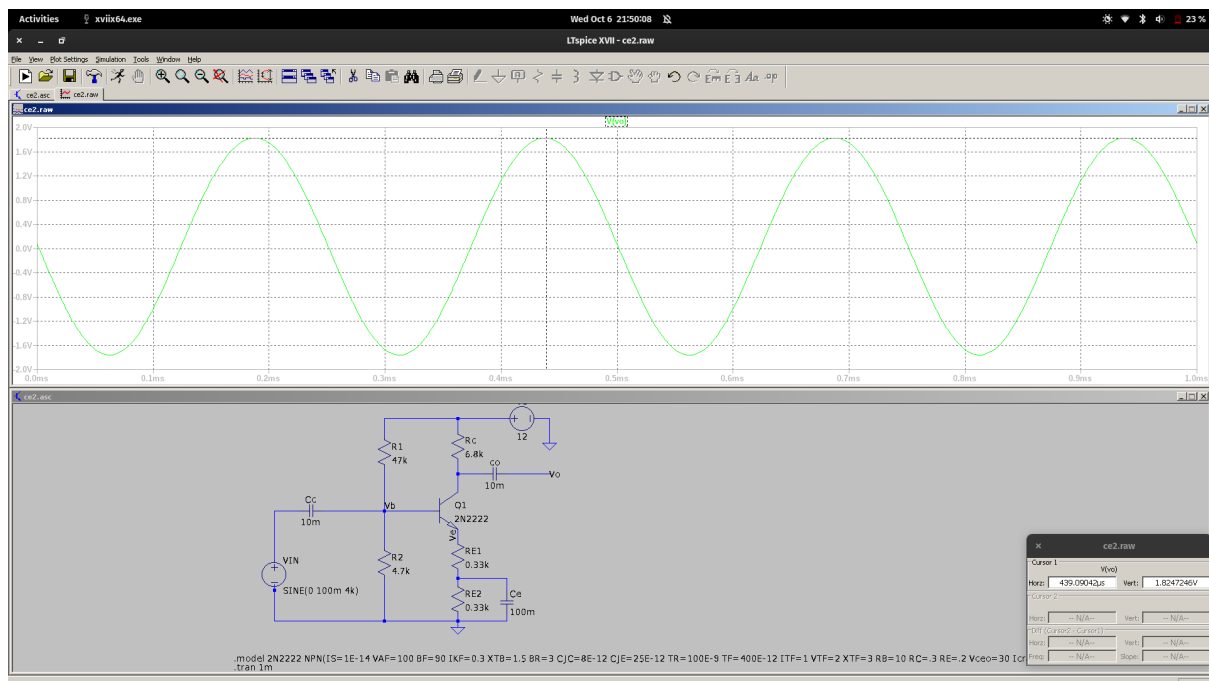

$V_o = 1.8247V$

Gain $A = V_o/V_i = 18.247$

b) $V_{in} = 0.2V$


Gain A = V_o/V_i = 16.84

c) $V_{in} = 0.3V$



Gain $A = V_o/V_i = 14.18$

d) $V_{in} = 0.45V$

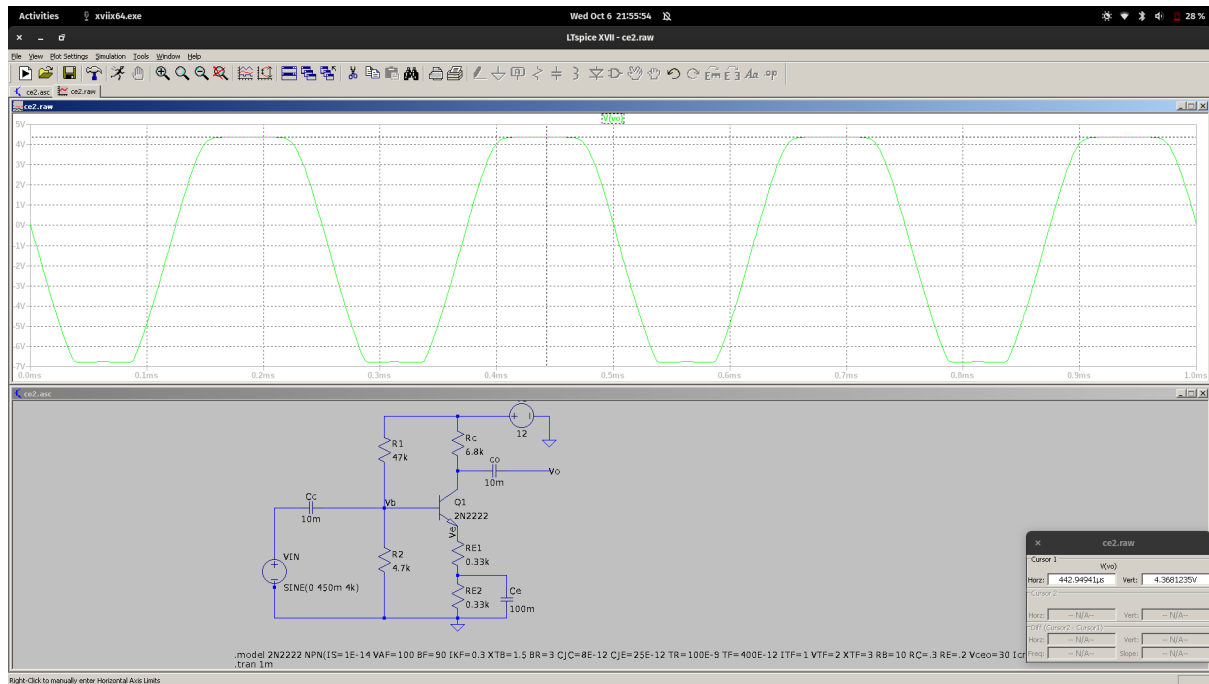


$V_o = 4.368V$

Gain $A = V_o/V_i = 9.706$

$V_{sm} = 0.45V$

2) With Load Resistance -


a) $V_{in} = 0.1V$

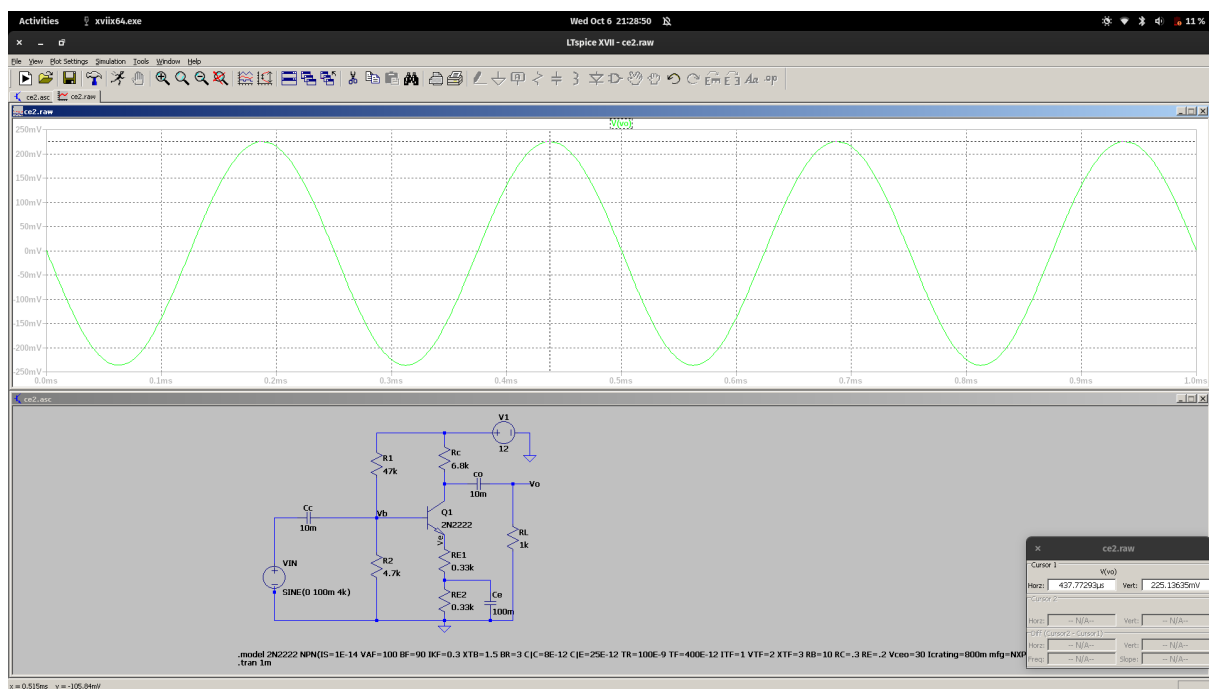

$$V_o = 225.136\text{mV}$$


$$\text{Gain } A = V_o/V_i = 2.251$$

$$\text{b) } V_{in} = 0.2\text{V}$$

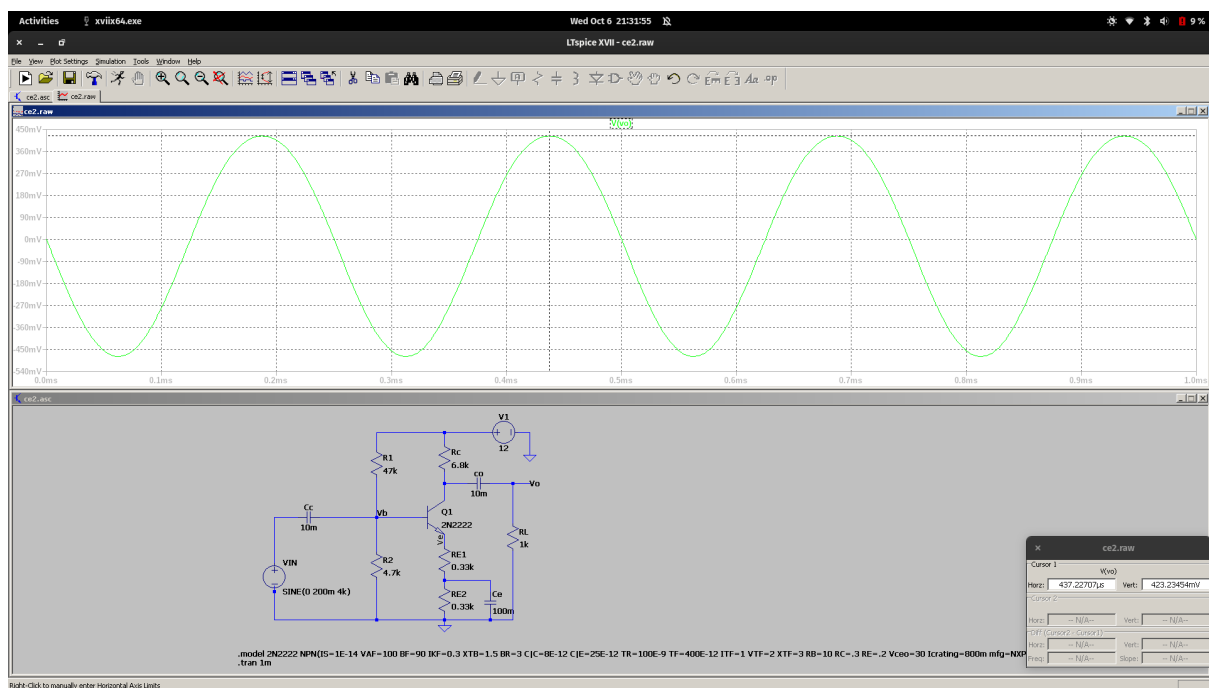

Gain A = V_o/V_i = 2.116


c) $V_{in} = 0.3V$

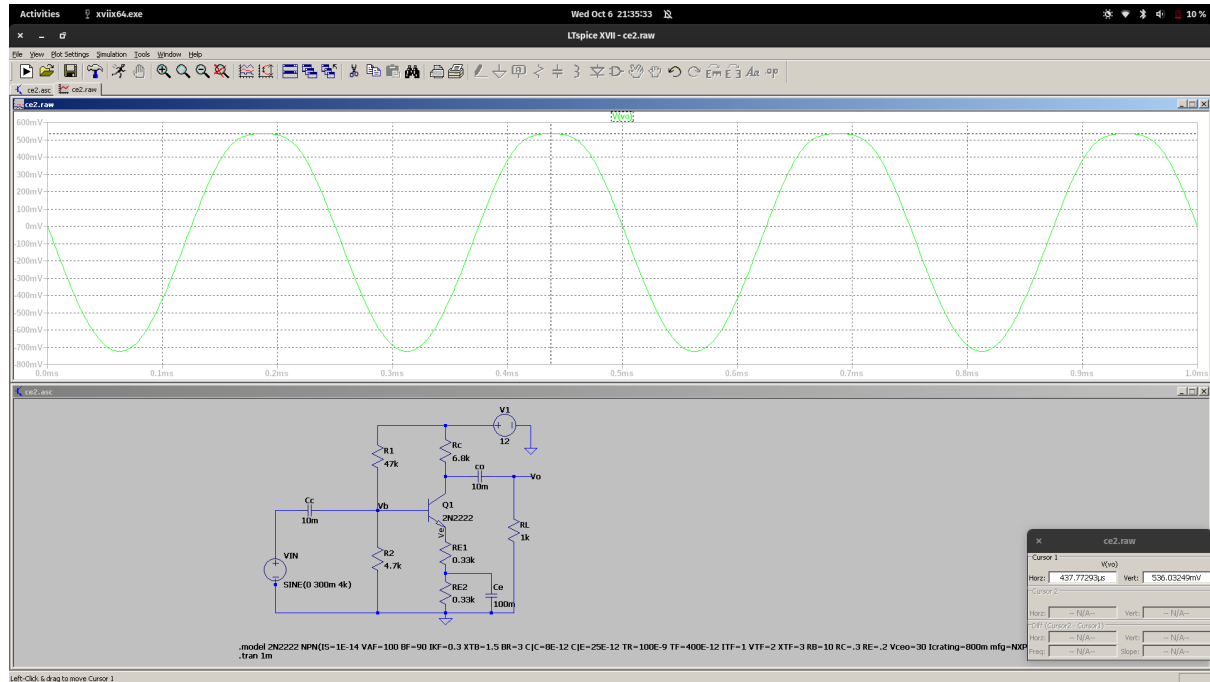

$$V_o = 536.032\text{mV}$$

Gain A = $V_o/V_i = 1.786$

d) $V_{in} = 0.35V$

 


$V_{sm} = 0.35V$

Vsm without RL is 0.45V and with RL is 0.35V. (Close by)


Measurement of Frequency Response

(i)

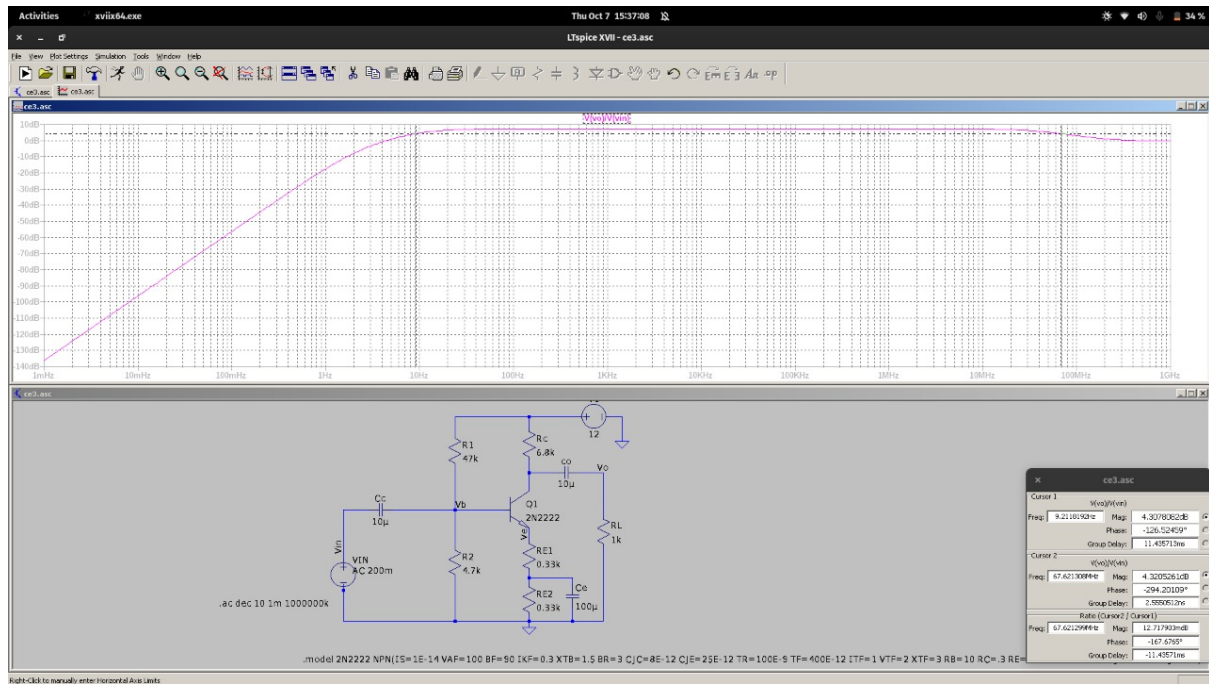

Low Cutoff Frequency = **9.211Hz**
 High Cutoff Frequency = **67.621MHz**

(ii) Load Disconnected

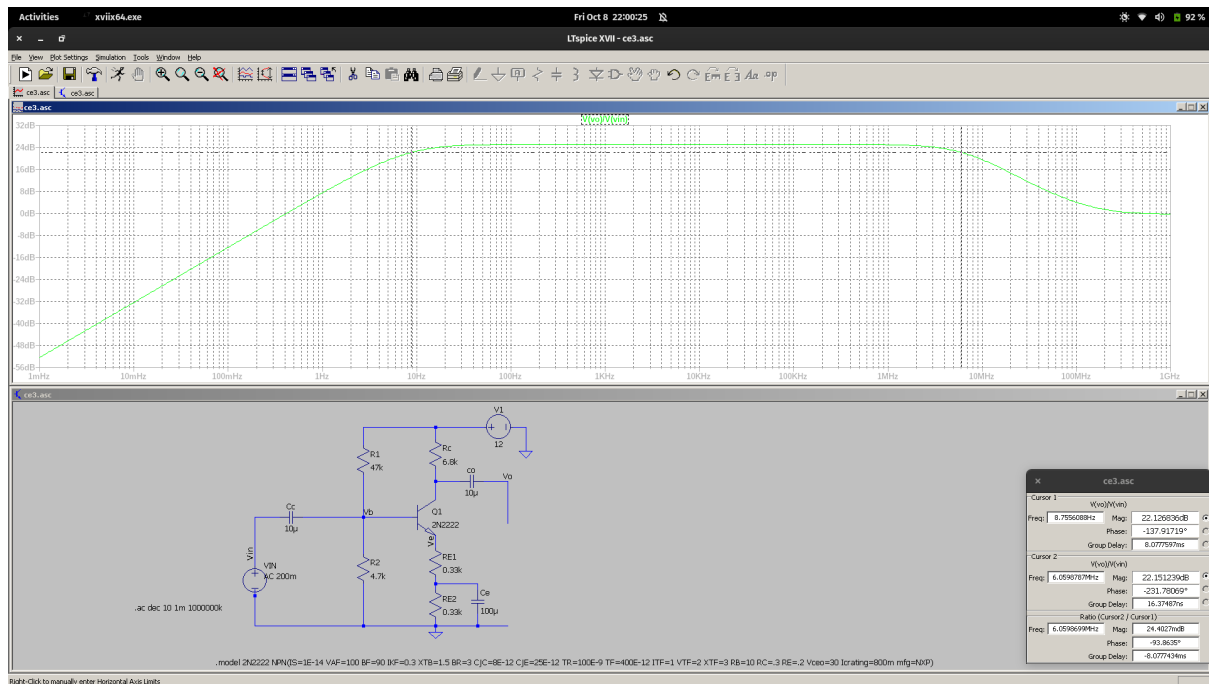


Low Cutoff Frequency = **8.755Hz**


High Cutoff Frequency = **6.059MHz**

From the above two(with and without load resistance), Low cutoff frequency is close by, but high cutoff frequency varies by 10x times.

(iii) Effect of C_e

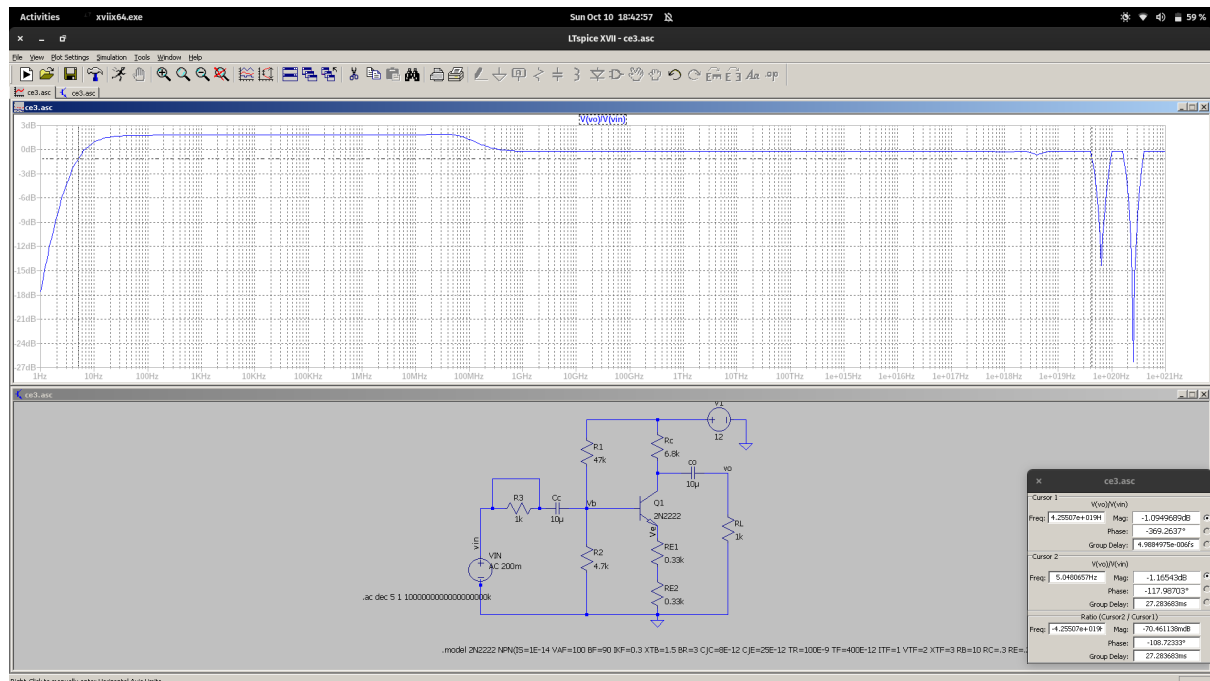

(iv) R_{e1} , R_{e2} fully biased

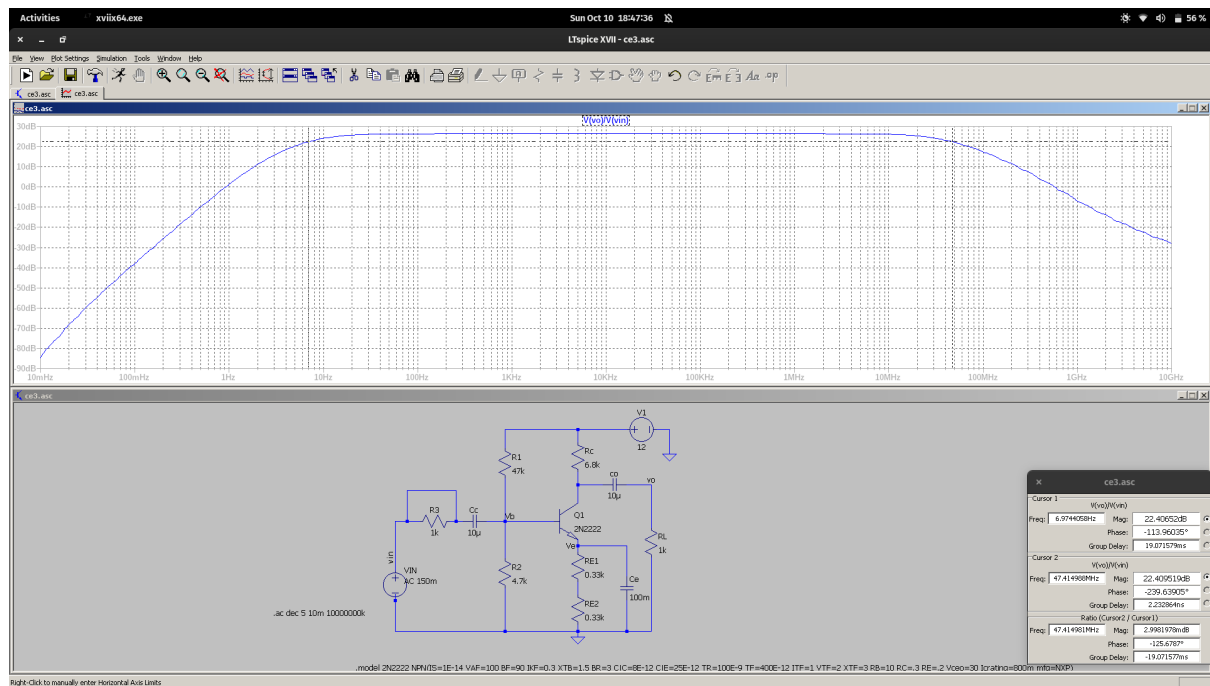


Low Cutoff Frequency = **6.974Hz**

High Cutoff Frequency = **47.414MHz**

Full Biasing of C_e leads high cutoff frequency to decrease drastically from 67.621MHz to 47.414MHz.

Output Resistance in the Mid-Frequency Range

 $R_L = 1K$, $V_{in} = 150mV$, $F = 100KHz$



Left-Click & drag to move Cursor 1

Vout | R(infinity) = 2.554V

Measurement of output resistance in mid-frequency range:-

$$V_{out/R_L} = 0.328V$$

$$f = 100 \text{ kHz}, R_L = 1k\Omega$$

$$V_{out/R_{\infty}} = 2.554V$$

$$V_{in} = 150 \text{ mV} < V_{SAT}$$

$$R_{out} = R_L \left(\frac{V_{out/R_{\infty}} - V_{out/R_L}}{V_{out/R_L}} \right)$$

$$= 1000 \left(\frac{2.554 - 0.328}{0.328} \right)$$

$$R_{out} = 6786.585 \Omega$$